
CS 223 Digital Design Section 01 Lab 04

NAME: Ferhat


SURNAME: Korkmaz

ID: 21901940

DATE: 08.04.2021

 

State	Transit		no bus	t put t	table
S ₂	5,	50	SA	82	S' S' S' LA, LAO LS, LSO
0	0	0	1	X	0 0 0 0 0 1 0
0	0	1	X	×	0 1 0 0 1 0
0	1	1	X	×	1001001
1	6	0	X	0	1011000
1	0	1	X	X	1101001
1	1	0	X	X	111010
1	1	1	1 x	K	0000110
$S_{0} = \overline{S}_{0} S_{1} + \overline{S}_{0} \overline{S}_{2} \overline{S}_{1} + \overline{S}_{0} S_{2} \overline{S}_{0}$ $L_{A_{0}} = S_{2} \oplus S_{1} + S_{1} \overline{S}_{0}$ $L_{A_{0}} = S_{0} (\overline{S}_{2} \oplus S_{1})$ $L_{B_{1}} = \overline{S}_{2} \oplus \overline{S}_{1} + S_{1} \overline{S}_{0}$ $L_{B_{0}} = S_{0} (\overline{S}_{2} \oplus \overline{S}_{1})$					

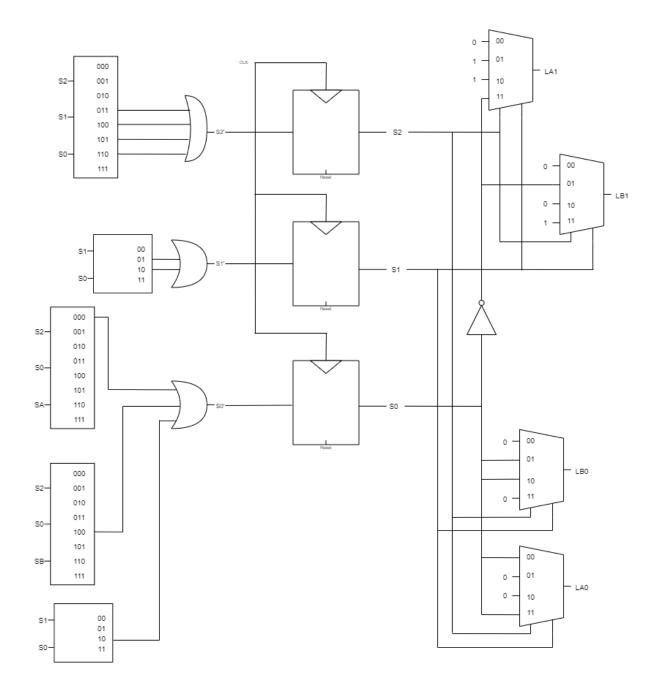

b-) 3 Flip-flops are needed in order to implement this problem since we have 8 states that are encoded as 3 bits.

c-)
module twoToFourDecoder(input logic input1, input0 ,output logic[3:0] myoutput);

assign myoutput[3] = input1 & input0; assign myoutput[2] = input1 & ~input0;

```
assign myoutput[1] = ~input1 & input0;
assign myoutput[0] = \sim \text{input} 1 \& \sim \text{input} 0;
endmodule
module fourToOneMux(input logic d0, d1, d2, d3, s0, s1, output logic y);
  assign y = s1? ( s0? d3: d2): ( s0? d1: d0);
endmodule
module threeToEightDecoder( input logic input2, input1, input0, output logic [7:0]
myoutput);
assign myoutput[0] = ~input2 & ~input1 & ~input0;
assign myoutput[1] = ~input2 & ~input1 & input0;
assign myoutput[2] = ~input2 & input1 & ~input0;
assign myoutput[3] = ~input2 & input1 & input0;
assign myoutput[4] = input2 & ~input1 & ~input0;
assign myoutput[5] = input2 & ~input1 & input0;
assign myoutput[6] = input2 & input1 & ~input0;
assign myoutput[7] = input2 & input1 & input0;
endmodule
module green(input logic[2:0] current_state, output logic [1:0] LA, LB);
  fourToOneMux assignLA0(current_state[0],0,0, current_state[0],
current_state[1],current_state[2], LA[0]);
  fourToOneMux assignLA1(0, 1, 1, ~current_state[0], current_state[1], current_state[2],
LA[1]);
  fourToOneMux assignLB0(0,current_state[0], current_state[0], 0, current_state[1],
current_state[2], LB[0]);
```

```
fourToOneMux assignLB1(1, ~current_state[0], 0, 1, current_state[1], current_state[2],
LB[1]);
endmodule
module blue(input logic SA, SB, input logic [2:0] state, output logic[2:0] nextstate);
  logic [3:0] n3;
  logic [7:0]n1, n2, n4;
  threeToEightDecoder s2next(~state[2], state[1], state[0], n4);
  twoToFourDecoder s1next(state[1], state[0], n3);
  threeToEightDecoder s0next(state[2], state[0],SA, n1);
  threeToEightDecoder sOnext2(state[2], state[0],SB, n2);
  twoToFourDecoder s0next3(state[1], state[0], n3);
  assign nextstate[0] = n1[0] | n2[4] | n3[2];
  assign nextstate[1] = n3[1] \mid n3[2];
  assign nextstate[2] = n4[0] |n4[1] | n4[2] | n4[7];
endmodule
module TrafficLightModule(input logic reset, clk, SA, SB,
               output logic [2:0] next_state, LA3, LB3
               );
typedef enum logic [2:0] {S0, S1, S2, S3, S4, S5, S6, S7} statetype;
logic [2:0] current_state;
//typedef enum logic [1:0] {red, yellow, green} lights;
logic [1:0] LA, LB;
blue firstcall(SA, SB, current_state, next_state);
DFlipFlop flop0(clk, reset, next_state[0], current_state[0]);
DFlipFlop flop1(clk, reset, next_state[1], current_state[1]);
DFlipFlop flop2(clk, reset, next_state[2], current_state[2]);
```

```
green secondcall(current_state, LA, LB);
```

```
assign LA3[2] = ~LA[1] & ~LA[0];
assign LA3[1] = \simLA[1];
assign LA3[0] = 1;
assign LB3[2] = \simLB[1] & \simLB[0];
assign LB3[1] = \simLB[1];
assign LB3[0] = 1;
endmodule
// Flip-flop D
module DFlipFlop(
       input clk, rst, d,
       output logic q);
 always@(posedge clk or posedge rst)
   if (rst)
    q \le 0;
   else
     q \ll d;
endmodule
```